

# LAB REPORT – 4

Name: Vanshita

Roll Number: 2021101102

Group: G6

## Aim of the experiment:


To design an Arithmetic and Logic Unit (ALU) capable of performing 8 Arithmetic/Logic functions on 1-bit operands as listed:


$F_2F_1F_0$	ALU Function	Y1	Y0
000	0(ZERO)	-	0
001	A OR B	-	$A + B$
010	A AND B	-	$A.B$
011	A EXOR B	-	$A \oplus B$
100	A PLUS B	Carry	Sum
101	A MINUS B	Borrow	Difference
110	A PLUS B PLUS C	Carry	Sum
111	A MINUS B MINUS C	Borrow	Difference

## Electronic components used:

1. Breadboards (2)
2. Small Breadboards (2)
3. Mini Breadboards (4)
4. Connecting Wires
5. LEDs (2)
6. Resistors (2)
7. Arduino UNO

Reference Diagram:

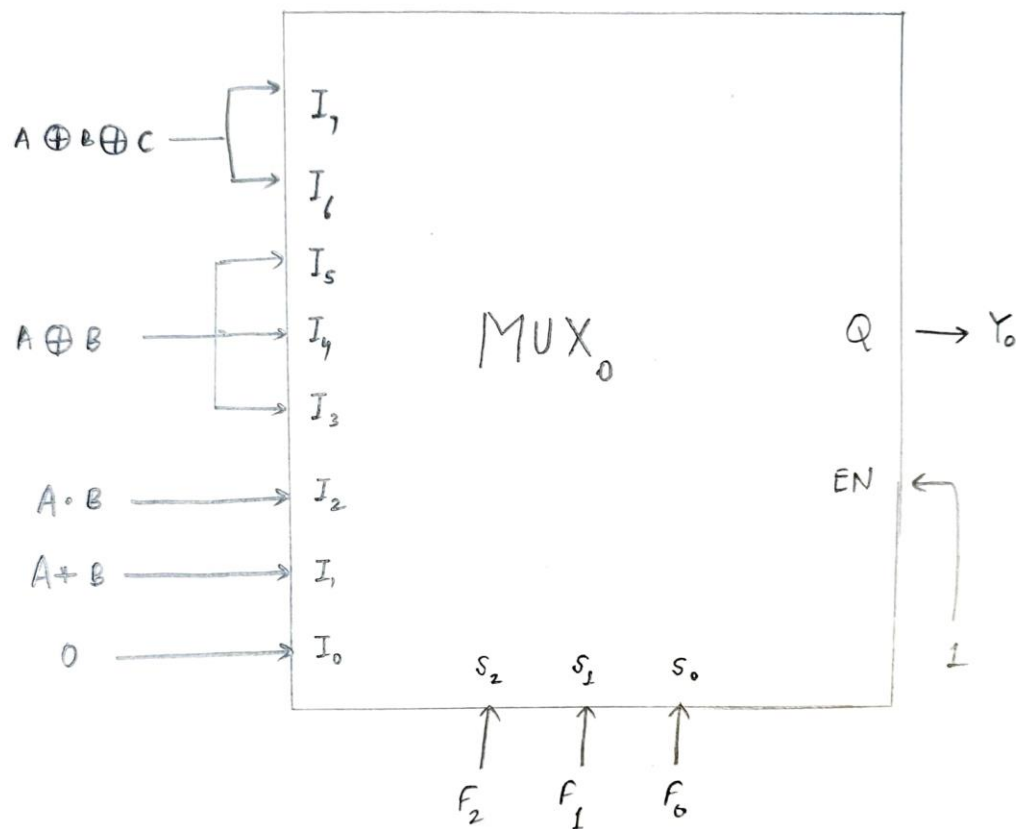

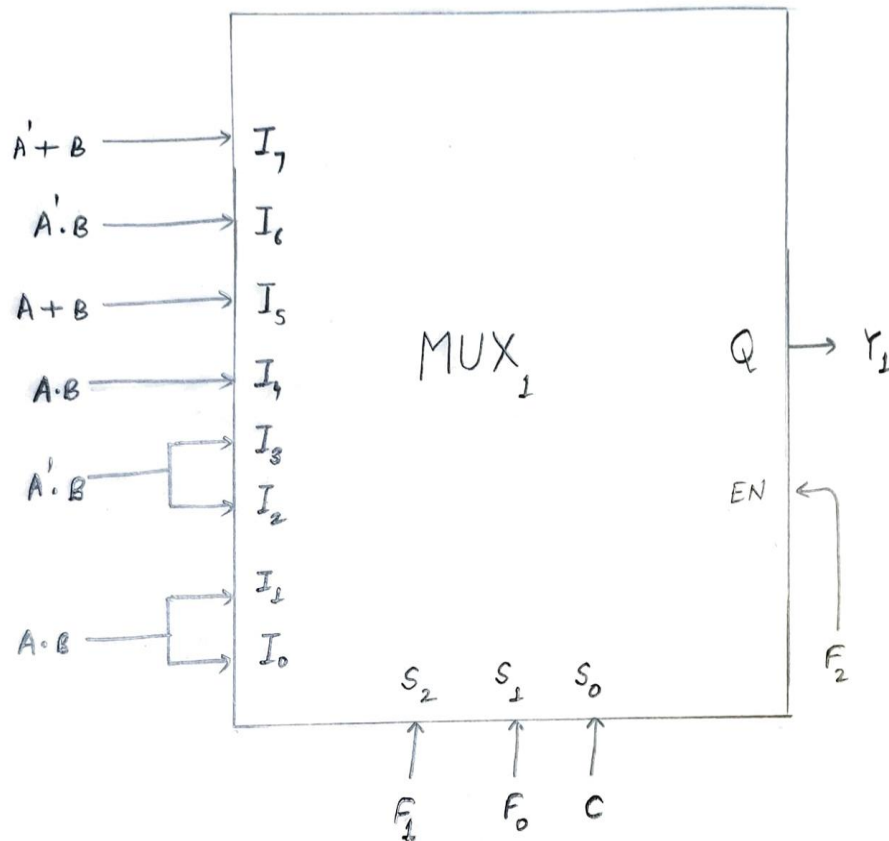

### Procedure:

1. Drag all the electronic components to the Tinkercad working area and set up the MUX circuit.
2. The final ALU output bits i.e., Y<sub>0</sub> and Y<sub>1</sub> will be generated by the two 8-input multiplexers – referred to as MUX 0 and MUX 1 respectively.
3. Note that MUX 0 is always enabled, while MUX 1 is enabled only when F<sub>2</sub>= 1 (for Arithmetic functions only).

This is because  $Y_1$  is required only to provide the CARRY/BORROW output for Arithmetic functions.

4. Verify that MUX0 and MUX1 generate the expected outputs  $Y_0$  and  $Y_1$  for different input lines.

Code:

```
int pin1 = 2;  
int pin2 = 3;  
int pin3 = 4;  
int pin4 = 11;  
int pin5 = 12;  
int pin6 = 13;  
int F2, F1, F0, A, B, C, k;
```

```
void setup()  
{  
  pinMode(pin1, OUTPUT);  
  pinMode(pin2, OUTPUT);  
  pinMode(pin3, OUTPUT);  
  pinMode(pin4, OUTPUT);  
  pinMode(pin5, OUTPUT);  
  pinMode(pin6, OUTPUT);  
  Serial.begin(9600);  
}
```

```
void loop()
{
  Serial.print("\nF2=");
  while(Serial.available()==0){}
  F2= Serial.read();
  F2= F2-'0';
  Serial.println(F2);
```

```
  Serial.print("F1=");
  while(Serial.available()==0){}
  F1= Serial.read();
  F1 = F1- '0';
  Serial.println(F1);
```

```
  Serial.print("F0=");
  while(Serial.available()==0){}
  F0= Serial.read();
  F0 = F0 - '0';
  Serial.println(F0);
```

```
  Serial.print("A=");
  while(Serial.available()==0){}
  A= Serial.read();
```

```
A = A - '0';
```

```
Serial.println(A);
```

```
Serial.print("B=");
```

```
while(Serial.available()==0){}
```

```
B= Serial.read();
```

```
B = B- '0';
```

```
Serial.println(B);
```

```
Serial.print("C=");
```

```
while(Serial.available()==0){}
```

```
C= Serial.read();
```

```
C = C - '0';
```

```
Serial.println(C);
```

```
digitalWrite(pin1, OUTPUT);
```

```
digitalWrite(pin2, OUTPUT);
```

```
digitalWrite(pin3, OUTPUT);
```

```
digitalWrite(pin4, OUTPUT);
```

```
digitalWrite(pin5, OUTPUT);
```

```
digitalWrite(pin6, OUTPUT);
```

```
Serial.print("Enter anything to go to read again");
```

```
while(Serial.available()==0){}
```

```
k=Serial.read();
```

```
}
```

Observation:

MUX<sub>0</sub>

F <sub>2</sub> F <sub>1</sub> F <sub>0</sub>	Output	Operation	ABC							
			000	001	010	011	100	101	110	111
000	I <sub>0</sub>	0	0	0	0	0	0	0	0	0
001	I <sub>1</sub>	A + B	0	0	1	1	1	1	1	1
010	I <sub>2</sub>	A . B	0	0	0	0	0	0	1	1
011	I <sub>3</sub>	$A \oplus B$	0	0	1	1	1	1	0	0
100	I <sub>4</sub>	$A \oplus B$	0	0	1	1	1	1	0	0
101	I <sub>5</sub>	$A \oplus B$	0	0	1	1	1	1	0	0
110	I <sub>6</sub>	$A \oplus B \oplus C$	0	1	1	0	1	0	0	1
111	I <sub>7</sub>	$A \oplus B \oplus C$	0	1	1	0	1	0	0	1

MUX<sub>1</sub>

F <sub>2</sub> F <sub>1</sub> F <sub>0</sub>	Output	ABC							
		000	001	010	011	100	101	110	111
000	I <sub>0</sub>	-	-	-	-	-	-	-	-

001	I <sub>1</sub>	-	-	-	-	-	-	-	-
010	I <sub>2</sub>	-	-	-	-	-	-	-	-
011	I <sub>3</sub>	-	-	-	-	-	-	-	-
100	I <sub>4</sub>	0	0	0	0	0	0	1	0
101	I <sub>5</sub>	0	0	1	1	0	0	0	0
110	I <sub>6</sub>	0	0	0	1	0	1	1	1
111	I <sub>7</sub>	0	1	1	1	0	0	0	1

### Conclusion:

Upon giving different inputs of  $F_2F_1F_0$  and ABC in the Tinkercad circuit, we see that the outputs match with those depicted in the truth table. Hence, the ALU is verified.

[Link for Tinkercad Simulation Circuit](#)